Lab Exercise 4: Seven Segment Display


Design and implement a Seven Segment Display with the functional description given below.

The aim of this exercise is to learn how to use 4-digit seven segment display available on the BASYS3 board. It involves designing and implementing a circuit to display 16-bit binary number set on the slide switches as a 4 digit hexadecimal number (number with base 16).


Let the 16-bit binary number be b_{15} b_{14} . . . b_1 b_0 and its hexadecimal equivalent be b_3 b_2 b_1 b_0 . Then these are related as follows.

$$\begin{aligned} &h_0 = b_3 b_2 b_1 b_0 \\ &h_1 = b_7 b_6 b_5 b_4 \\ &h_2 = b_{11} \ b_{10} \ b_9 b_8 \\ &h_3 = b_{15} \ b_{14} \ b_{13} \ b_{12} \end{aligned}$$

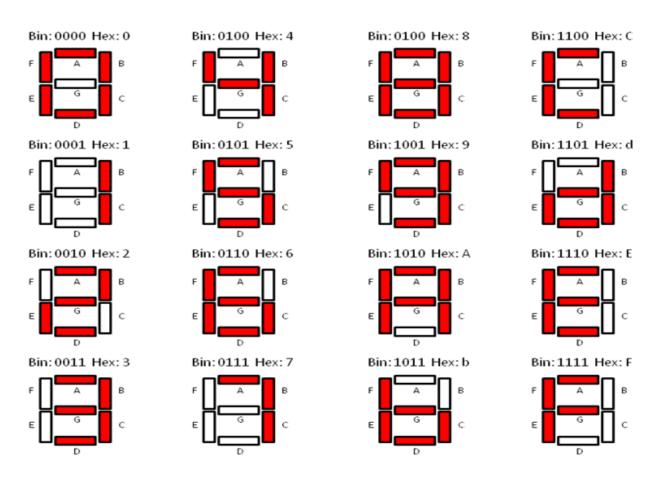Instructions on how to use the display are given in section 8 of the BASYS3 board reference manual (available on Moodle). Patterns to be used for displaying hexadecimal digits are shown in the figure below.



A rough sketch of the circuit is shown below. The 4 digits are displayed in a time multiplexed manner with refresh rate in the range of 60 Hz to 1 KHz. The clock available on the FPGA board has a frequency of 100 MHz which needs to be suitably divided to get a clock in the required range (4 times the refresh rate, that is, from 240 Hz to 4 KHz). However, during simulation, it is convenient to work directly with the clock without dividing it. Therefore, the circuit should provide two modes – one where the clock is divided (slow clock mode) and the other where it is not (fast clock mode).

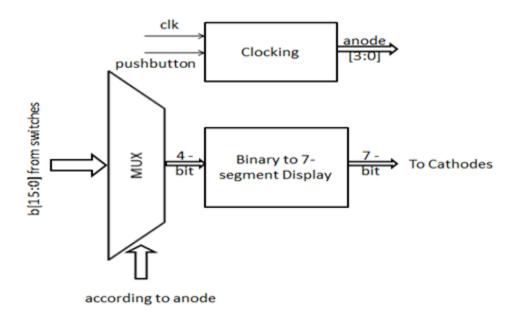

Refer Basys 3 Document (part 8) for enabling cathodes and anodes.



b[15:0] is the bit vector for 16 bit input. pushbutton is used to select clock rate.

pushbutton = 1 selects the fast clock mode. For Simulation pushbutton = 0 selects the slow clock mode. For Synthesis For verifying the synthesized circuit board, do not press pushbutton.

cathode[0] corresponds to A segment and cathode[6] corresponds to G segment.

Pin Name	Description	Purpose
clk	Input (from Basys 3 Internal clock)	clocking
b[15:0]	Input	Binary input from switches
pushbutton	Input	Selects clock rate
anode[3:0]	Output	To enable the digit on Display
cathode[6:0]	Output	To display the Hex Digit

Top Level Module Name: lab4_seven_segment_display